

## End Semester Examination – Winter 2018

**Course: B. Tech. in Electronics and Telecommunication Engineering**

**Subject Name: Digital Logic design**

**Max Marks: 60**

**Sem: III**


**Subject Code: BTEXC305**

**Duration: 3 Hr.**

***Instructions to the Students:***

1. The level question/expected answer as per OBE or the Course Outcome (CO) on which the question is based is mentioned in ( ) in front of the question.
2. Use of non-programmable scientific calculators is allowed.
3. Assume suitable data wherever necessary and mention it clearly.

		(COs)	Marks
<b>Q. 1</b>	A) Simplify following expression using K-Map $f(A,B,C,D) = \sum m(1,4,7,12,13, 14,15) + d(0, 5, 8)$	(1,2)	06
	B) Implement following using multiplexer	(1,2)	06
	(a) Half-adder (b) Half-subtractor		
<b>Q. 2</b>	A) Design 3-bit synchronous up counter using JK flip flop.	(2,3)	06
	B) Draw and explain Universal shift Register.	(2,3)	06
<b>Q. 3</b>	Draw state diagram for given sequential circuit shown in figure 1.	(2,3)	12

 

<b>Q.4</b>	A)	Define and explain: i) Fan in and Fan out    ii) Noise immunity    iii) Propagation Delay	(2)	06
	B)	Explain in brief the operation of CMOS NAND Gate with schematic diagram.	(2)	06
<b>Q5.</b>	A)	Implement given Boolean functions using PLA, PAL and PROM $F1(A,B,C) = \sum m(0, 2, 6, 7)$ $F2(A,B,C) = \sum m(1, 3, 4, 5, 7)$	(2,3)	06
	B)	Write VHDL code for Mux 4:1 using dataflow and behavioural architecture style.	(4)	06
	<b>Q6.</b>	A) Draw combinational circuit for Binary Parallel Adder and Subtractor.	(3)	06
	B)	Draw Asynchronous 4 bit up counter with clock waveform.	(2,3)	06

\*\*\*\*\*The End\*\*\*\*\*