

**DR. BABASAHEB AMBEDKAR TECHNOLOGICAL UNIVERSITY, LONERE**  
**End Semester Examination – Winter 2018**

**Course:** B. Tech in E&TC

**Subject Name:** Analog Circuits

**Date:** 03/12/2018

**Sem:** III

**Subject Code:** BTEXC302

**Duration:** 3 Hrs.

**Max Marks:**60

**Instructions to the Students:**

1. Solve **ANY FIVE** questions out of the following.
2. The level question/expected answer as per OBE or the Course Outcome (CO) on which the question is based is mentioned in ( ) in front of the question.
3. Use of non-programmable scientific calculators is allowed.
4. Assume suitable data wherever necessary and mention it clearly.

|   | (Level/CO)        | Marks     |
|---|-------------------|-----------|
| <b>Q. 1</b> Solve the following.  |                   |           |
| A) Explain Block diagram of OPAMP   | <b>Understand</b> | <b>06</b> |
| B) Write Short note on Current Mirror Circuit   | <b>Remember</b>   | <b>06</b> |
| <b>Q.2</b> Solve the following.   |                   |           |
| A) Design the OPAMP circuit which can give the output as $V_o = 2V_1 - 3V_2 + 4V_3 - 5V_4$    | <b>Evaluate</b>   | <b>06</b> |
| B) Draw circuit diagram of Instrumentation Amplifier and Derive expression for output voltage | <b>Synthesize</b> | <b>06</b> |
| <b>Q. 3</b> Solve the following.  |                   |           |
| A) Draw and Explain circuit diagram of Full Wave Precision Rectifier with its operation       | <b>Understand</b> | <b>06</b> |
| B) Compare Schmitt Trigger and Comparator   | <b>Understand</b> | <b>06</b> |
| <b>Q.4</b> Solve Any Two of the following.  |                   |           |
| A) Write short note on I to V Converter   | <b>Remember</b>   | <b>06</b> |
| B) Draw and Explain R-2R Ladder DAC   | <b>Understand</b> | <b>06</b> |
| C) Draw and Explain Dual Slope ADC  | <b>Understand</b> | <b>06</b> |
| <b>Q. 5</b> Solve the following.  |                   |           |
| A) Compare RC Phase Shift Oscillator and Wien Bridge Oscillator                               | <b>Understand</b> | <b>06</b> |
| B) Design Wien Bridge Oscillator circuit to have output frequency of 10KHz                    | <b>Evaluate</b>   | <b>06</b> |
| <b>Q. 6</b> Solve the following.  |                   |           |
| A) Draw and Explain Block Diagram of PLL  | <b>Understand</b> | <b>06</b> |
| B) Draw and Explain Band Pass Filter circuit and its Frequency response                       | <b>Understand</b> | <b>06</b> |

\*\*\* End \*\*\*